



ASSIGNMENT REPORT

Computer Architecture (3EC503CC24)

TOP – IMPLEMENTING AND SIMULATING RISC-V PROCESSOR SINGLE CYCLE
CORE AND CACHE

MADE BY – VARUN LUTHARIA AND ARYAN SAHAL

ROLL NUMBER – 22BEC069 AND 23BEC502

BATCH – A2

Implementing and Simulating RISC-V Processor and Cache

Varun Lutharia and Aryan Sahal

Department of Electronics & Communication, Institute of Technology

Nirma University, Ahmedabad, Gujarat-382481, India

22bec069@nirmauni.ac.in and 23bec502@nirmauni.ac.in

Abstract – RISC-V processors are widely used in range of devices such as Microcontrollers and IOT, FPGA and Consumer Electronics. It comprises of several unit as such as Program Counter, Program Counter + 4 (With help of Adder block), 3 Muxes, Register Module, Control Unit, ALU Block, Instruction Memory and several others etc. Firstly, as we know processor always uses to get execute as in fetch, decode, execute so instruction program counter will fetch thereafter it gets executed while being getting executed Program Counter will fetch the instruction present next in Instruction Memory. Some Instruction such as LW, SW are there present in Cache (as Instruction Cache) always instructions which is going to be executed will check that if it's equal to SW or LW then hit occurs, else miss occurs as miss happened instruction needed to be fetched from instruction memory there are Various module present such as PC, PC+4, Mux, Control Unit, Instruction Memory, Register Module, Immediate generator Module, ALU Control, ALU Result, Data Memory, Cache Module etc.

Keywords – Program Counter, Program Counter + 4, Types of Instruction, Pipelining Mechanism, Immediate Generator Module Block etc.

Literature Survey – With the growing demand for open-source processor architectures, RISC-V has emerged as a widely adopted instruction set architecture (ISA). Efficient cache memory design is crucial for optimizing RISC-V processor performance, reducing memory access latency, and improving power efficiency. Unlike other processors such as 8086, ARM, RISC-V is open-source with the help of which one can do as much as modification for project related work and also required instruction which user do wants, simplified decoding making hardware complexity lesser and even Power Consumption Supported by major compilers such as (Spike, Qemu, LLVM, GCC), operating systems (Linux, FreeBSD, Zephyr).

This report mainly discusses how to use Verilog HDL in such a manner such that we can Implement RISC-V Processor Cache, Chip used to realize this Project is Cyclone II EP2C35F672C6.

Limitations of the currently available technology – There are few limitations for Implementing and Simulating RISC-V Processor and Cache with currently available Technology.

1. Limited Standardization in RISC-V Cache Implementations

- Unlike ARM and x86, which have well-established cache architectures present, RISC-V does not have a single standard cache implementation.
- Different RISC-V vendors need to implement their own cache architecture, leading to compatibility issues in simulation and hardware deployment finding that part difficult.

2. FPGA Implementation Constraints

- Implementing a high-performance RISC-V cache on an FPGA is challenging due to limited on-chip memory and bandwidth along with we can't do performance measure thoroughly we can only do miss or hit rate not like we can do benchmark performance over here only with help of Verilog Code we can't do so.
- Cache coherence mechanisms for multi-core RISC-V processors on FPGA are still being underdeveloped.

Proposed Solution – Limitations Present can be overcome through Following Work

Cache Subsystem Abstraction Layers:

- Some projects have proposed an abstraction layer between the cache and processor, allowing modular plug-and-play cache architectures.
- This would enable different cache architectures to be integrated without significant software changes.

Hybrid Benchmarking Approaches: Since full benchmarking is difficult on FPGA Several Solutions are listed below:

- **Software-Based Profiling (gem5, Spike)** to test various cache configurations before FPGA deployment.
- **Hardware-Based Miss/Hit Rate Analysis** for verifying cache efficiency in FPGA.
- **Performance Counters Integration** (like RISC-V performance monitoring extensions) to extract meaningful performance metrics from FPGA designs.

BLOCK DIAGRAM

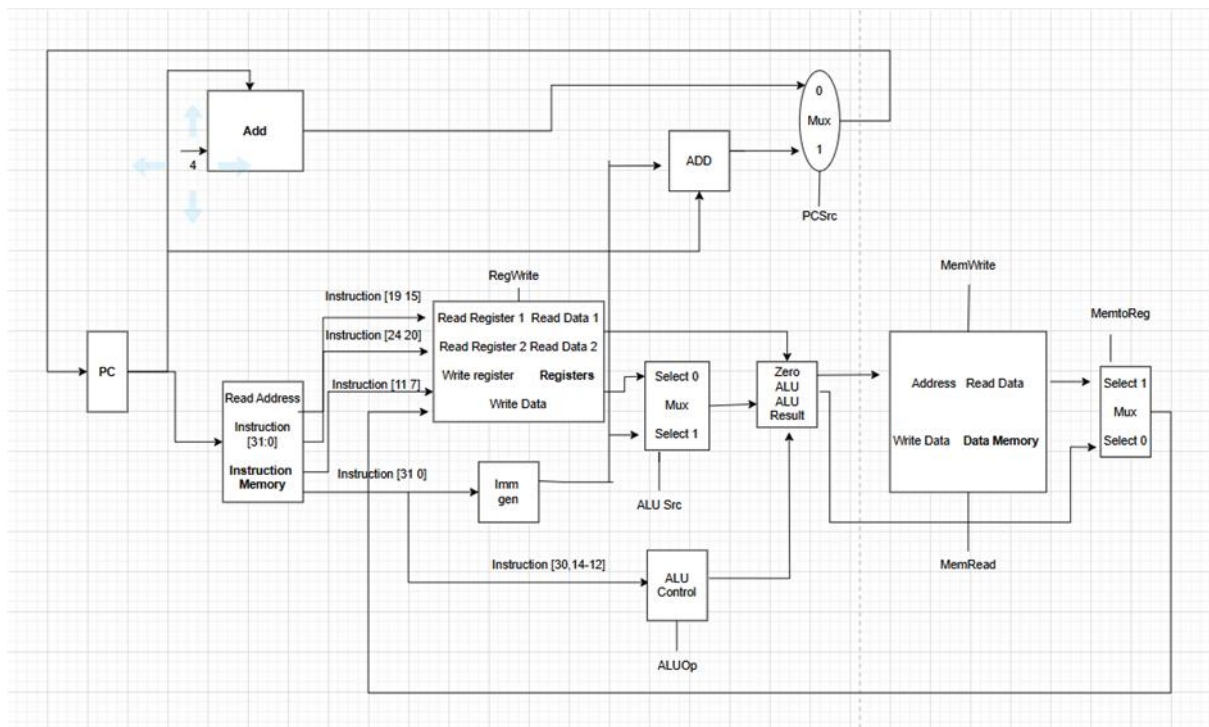


Fig. 1 Block Diagram of RISC-V Processor and Cache

SIMULATION RESULTS

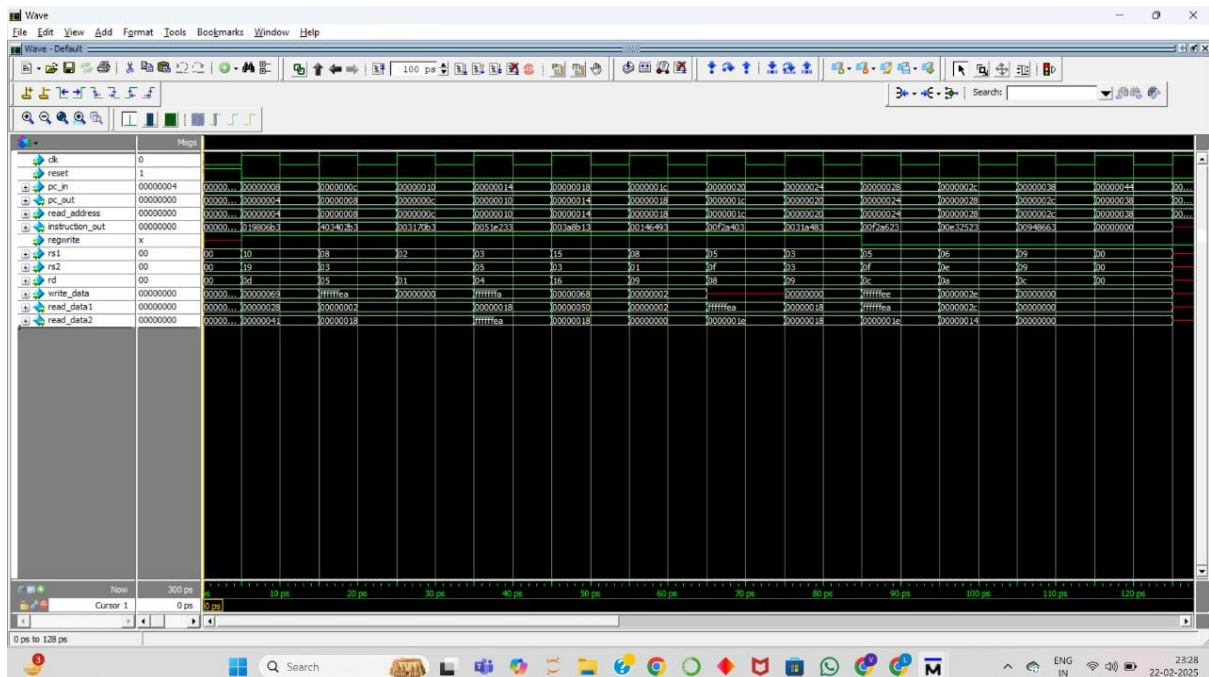


Fig. 1 RTL Simulation Waveform

 


Fig.2 RTL Simulation Waveform

 


Fig.3 RTL Waveform Simulation

Analysis of the obtained results

So, Values of registers are respectively associated in the code, along with that in code itself we had constructed several instructions (12), in Instruction memory they are written step by step they will get executed with each clock cycle and obtained result aligned with expected results either of any instruction lw, sw, add, sub or any etc.

Any other relevant information

RTL Synthesis of RISC-V Processor

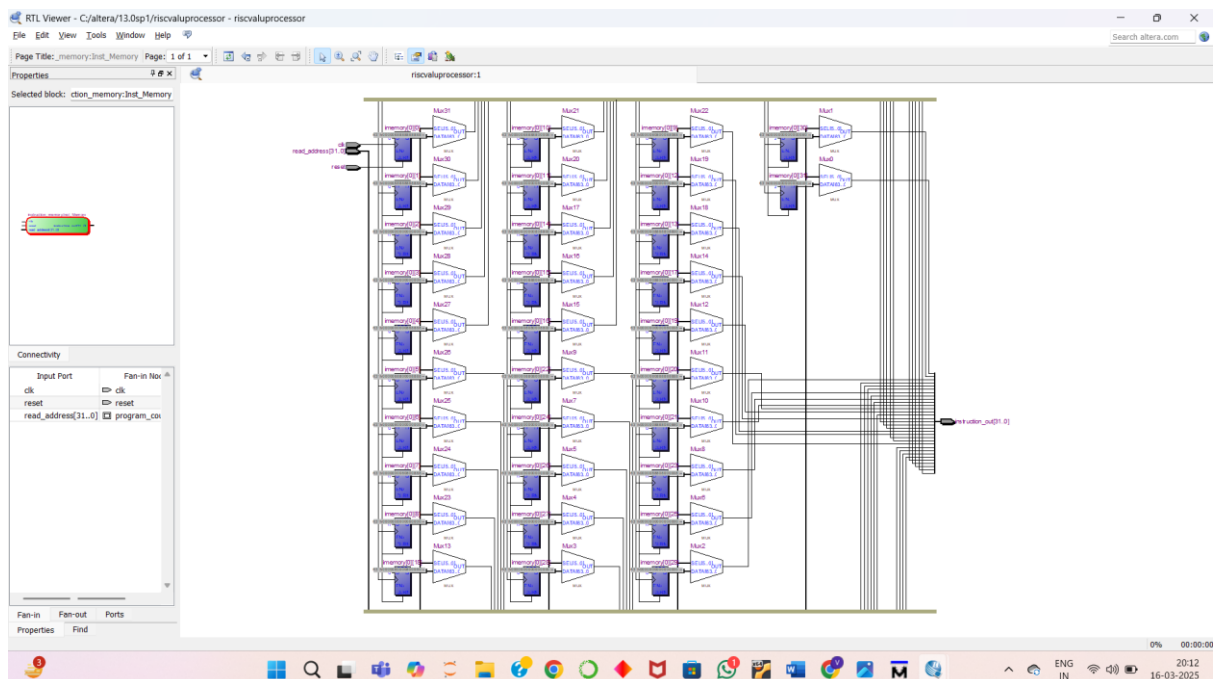


Fig. 3 RTL of Instruction Memory

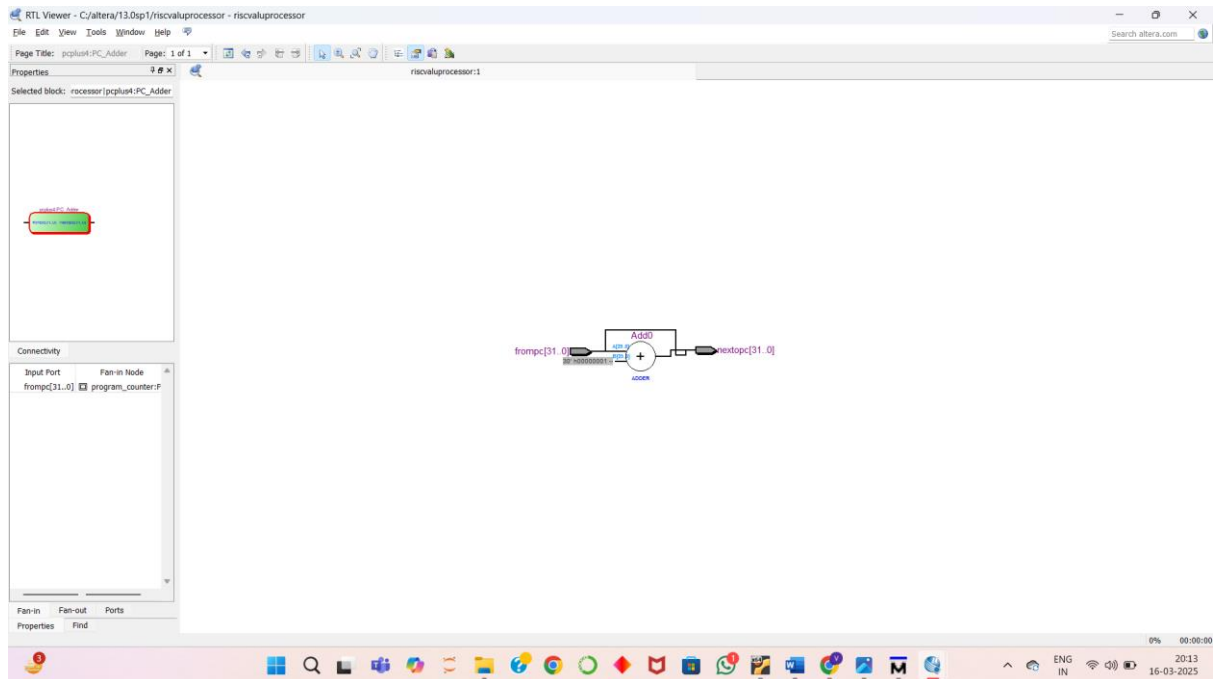


Fig. 4 RTL of PC Adder

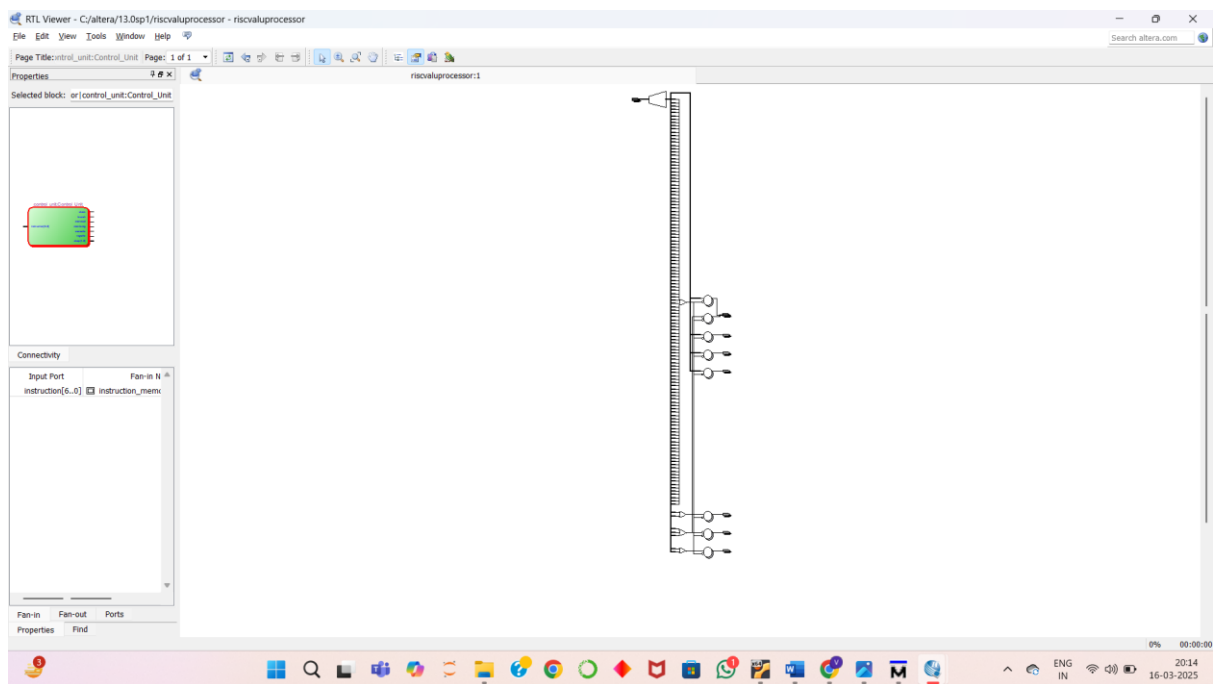


Fig. 5 RTL of Control Unit

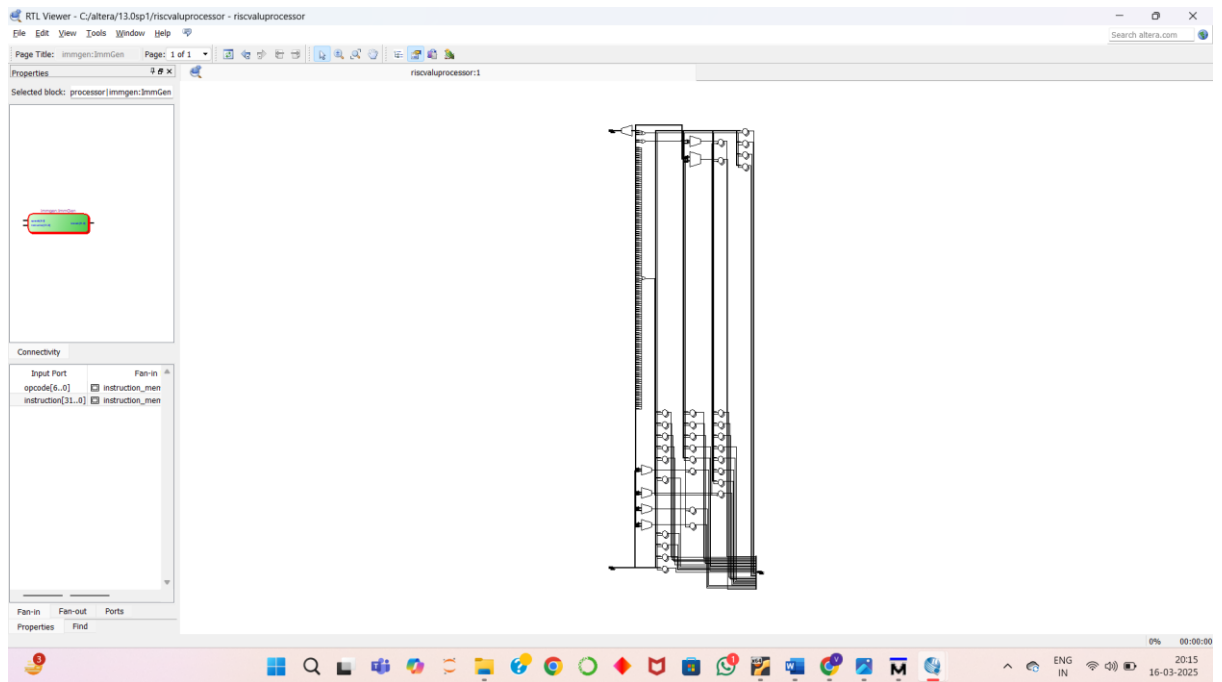


Fig. 6 RTL of Instruction Memory.

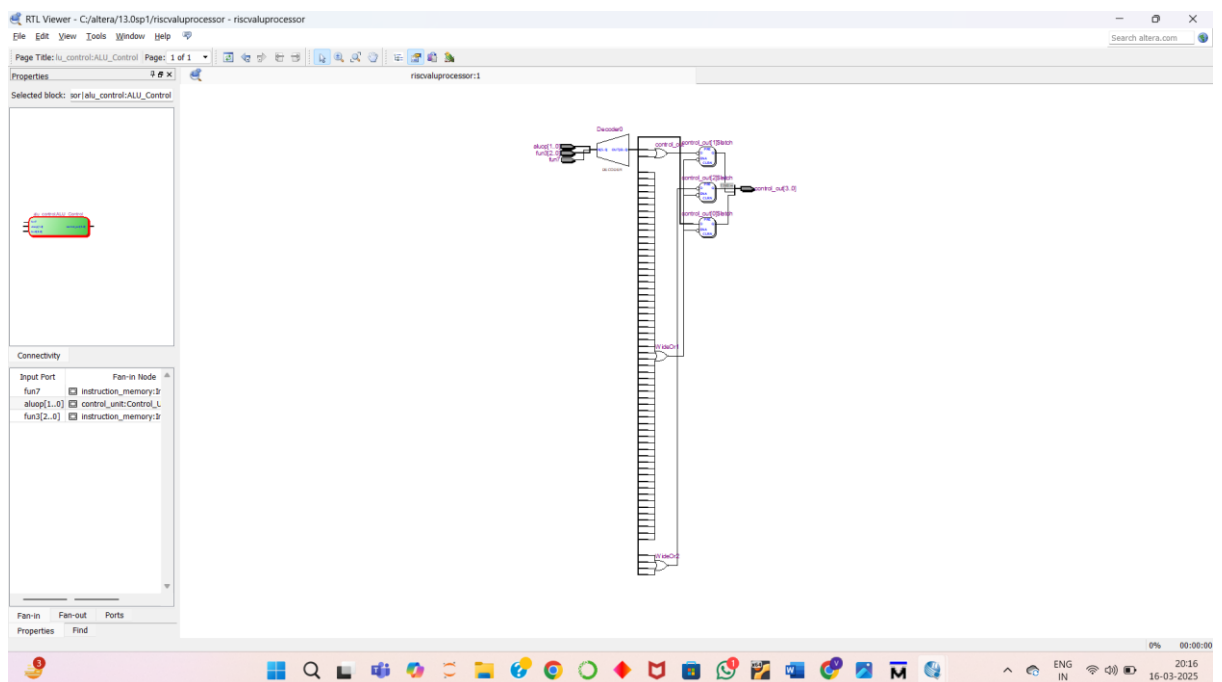


Fig. 7 RTL of ALU Control Unit.

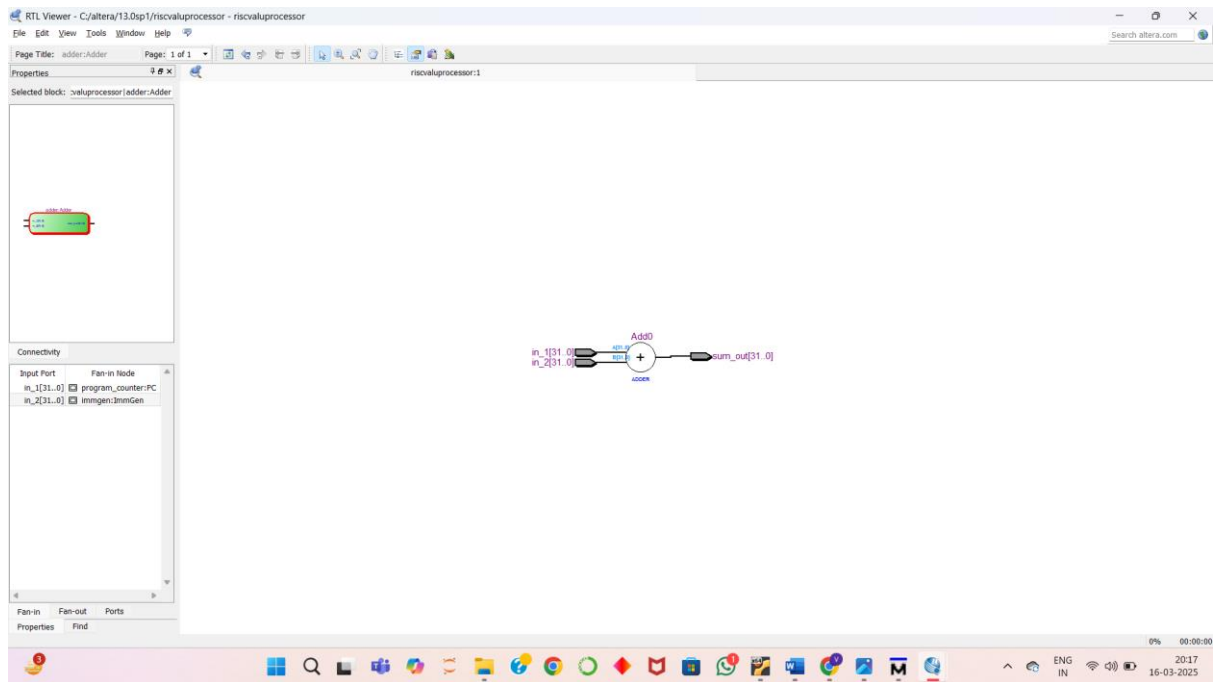


Fig. 8 RTL of Adder.

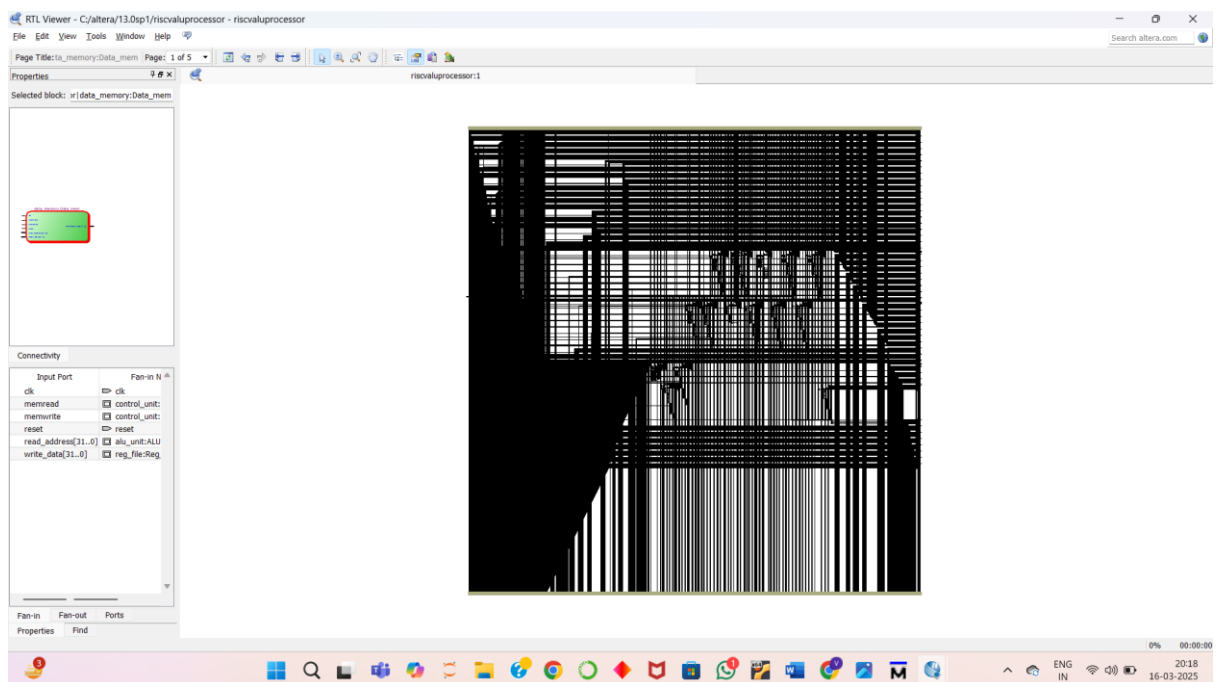


Fig. 9 RTL of Data Memory.

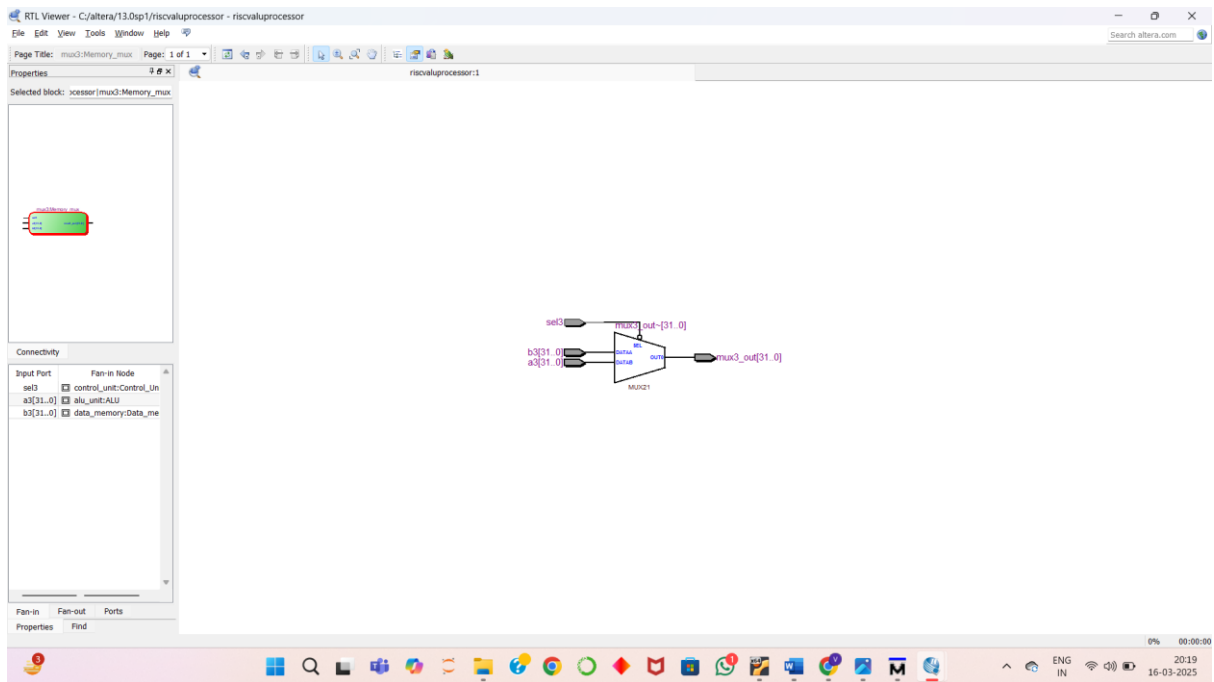


Fig. 10 RTL of Memory Mux.

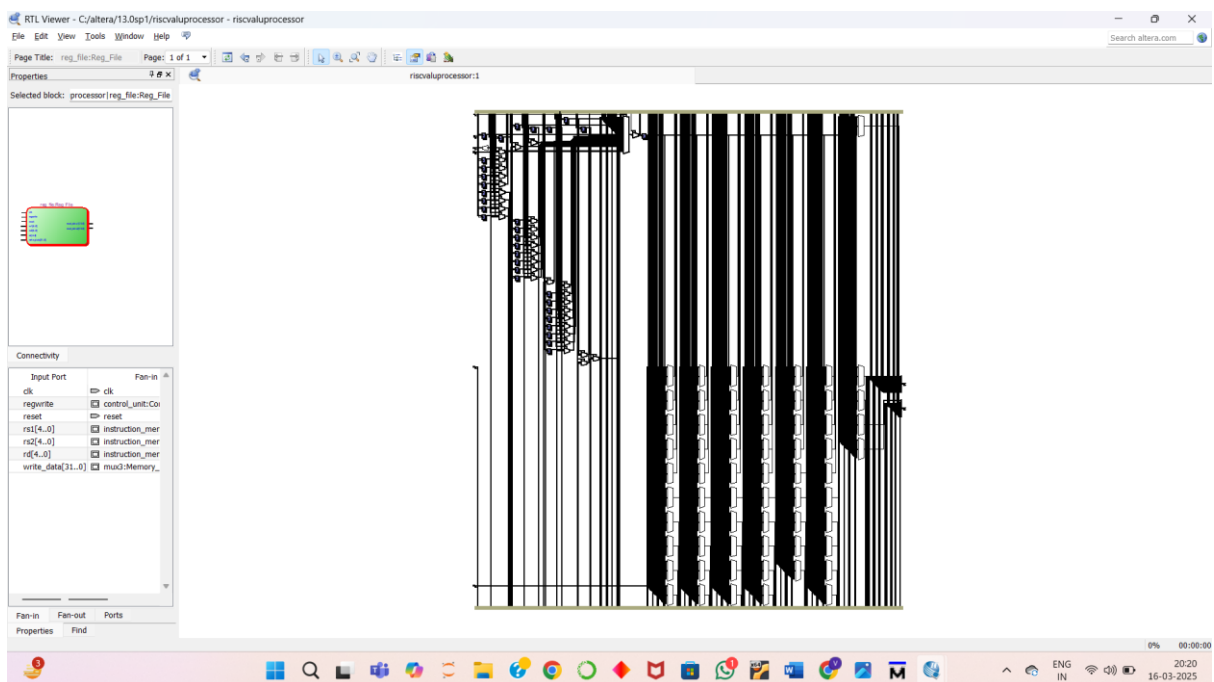


Fig. 11 RTL of Register Memory.

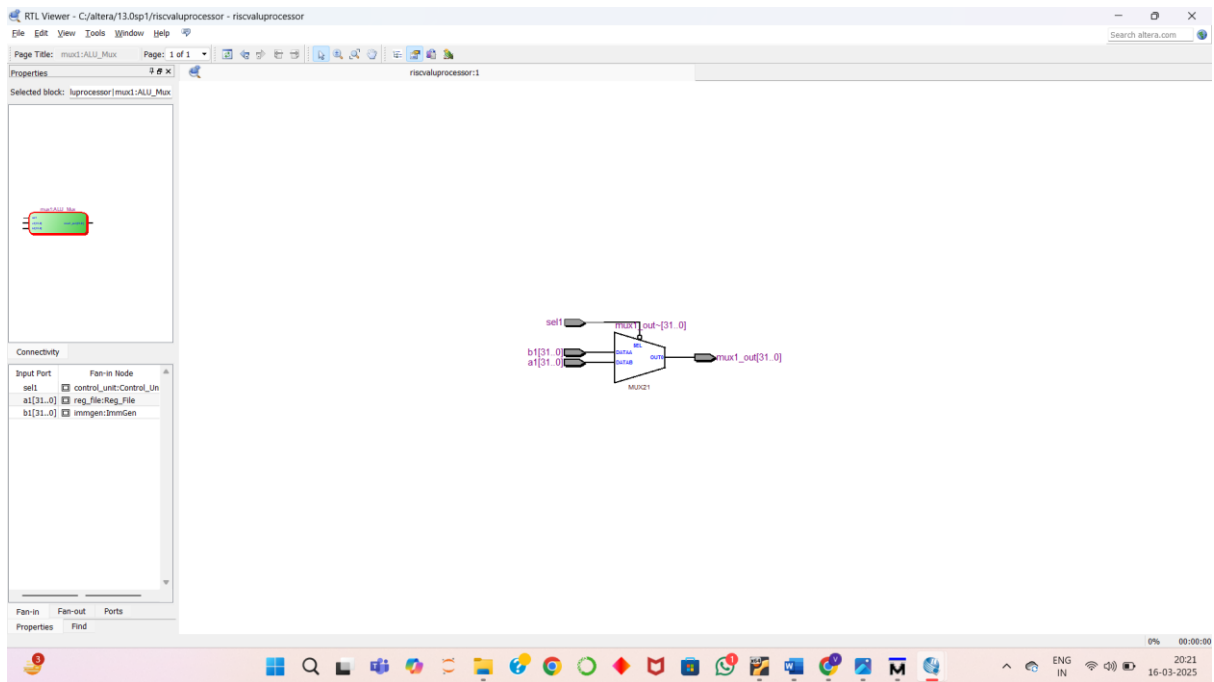


Fig. 12 RTL of ALU Mux.

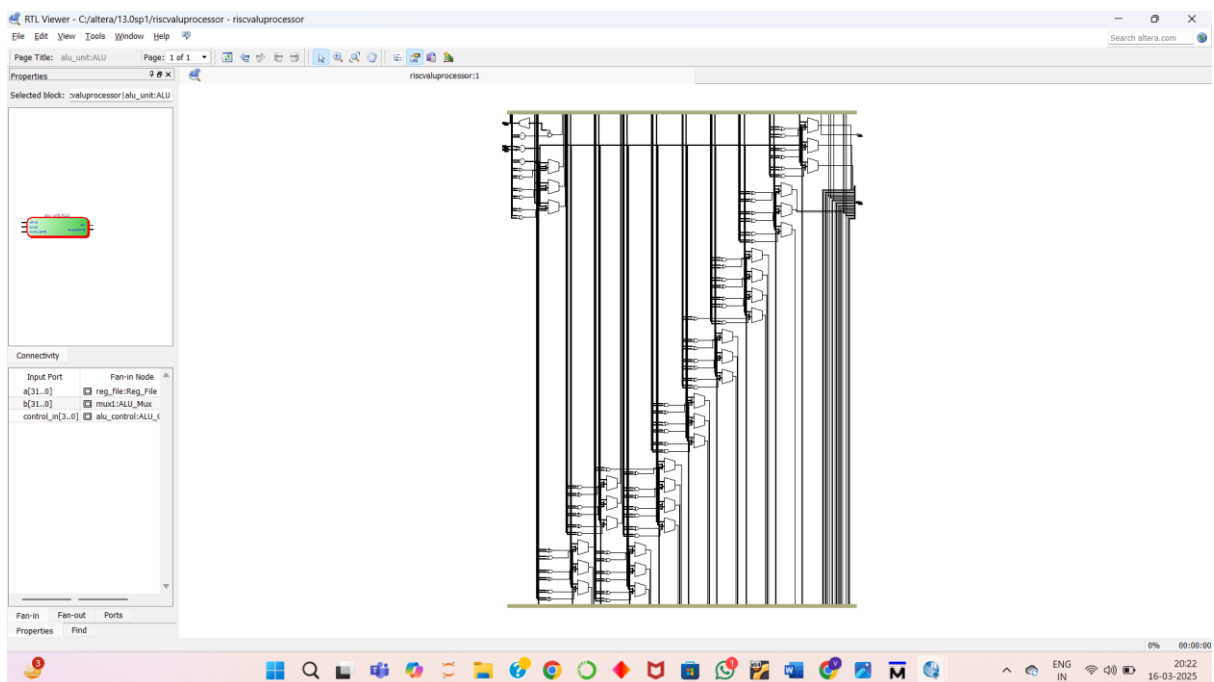


Fig. 13 RTL of ALU Unit.

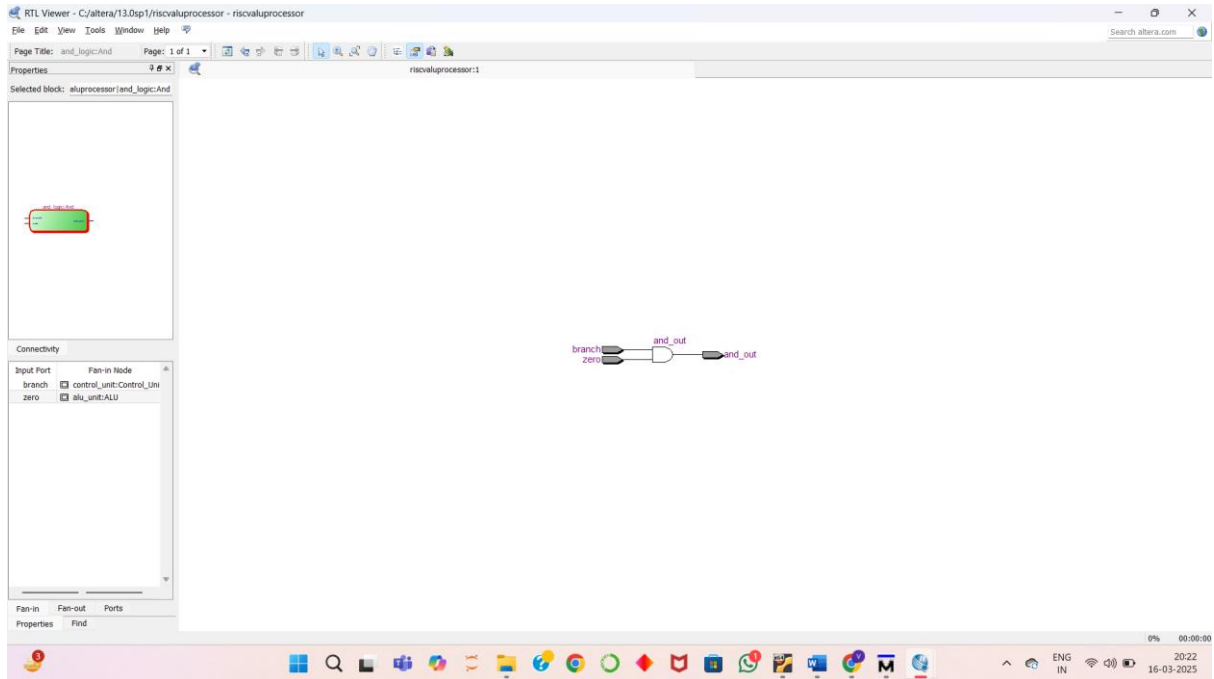


Fig. 14 RTL Unit of AND out.

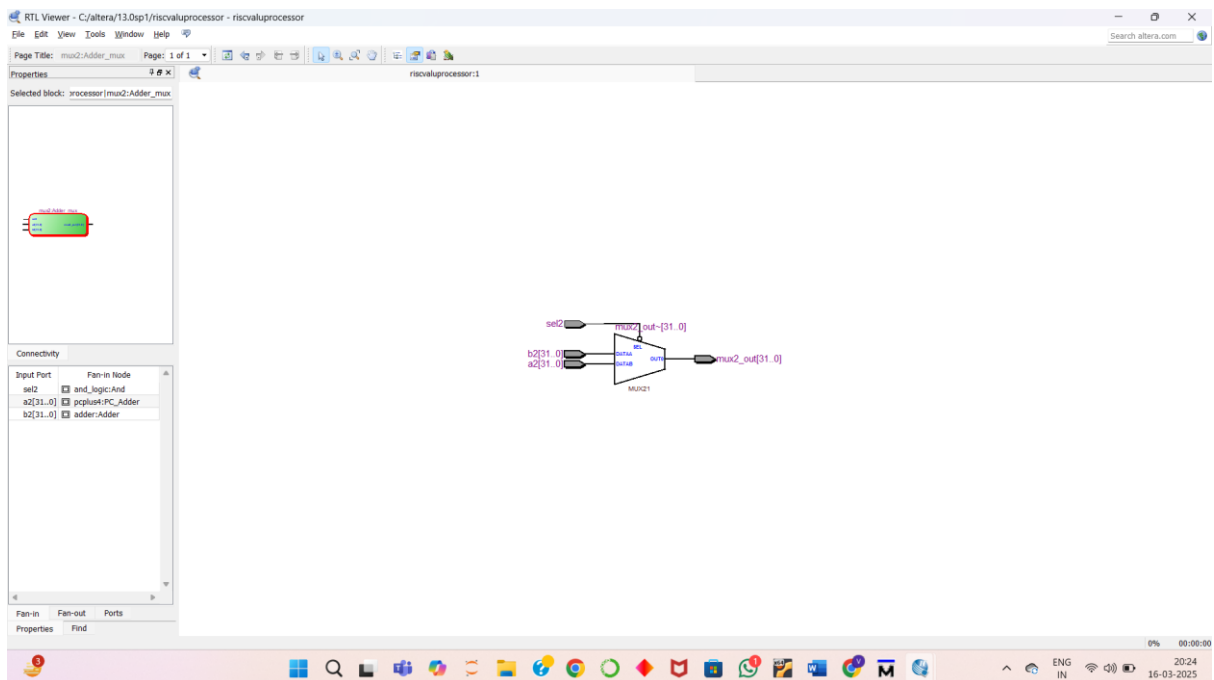


Fig. 15 RTL Unit of ADDER Mux.

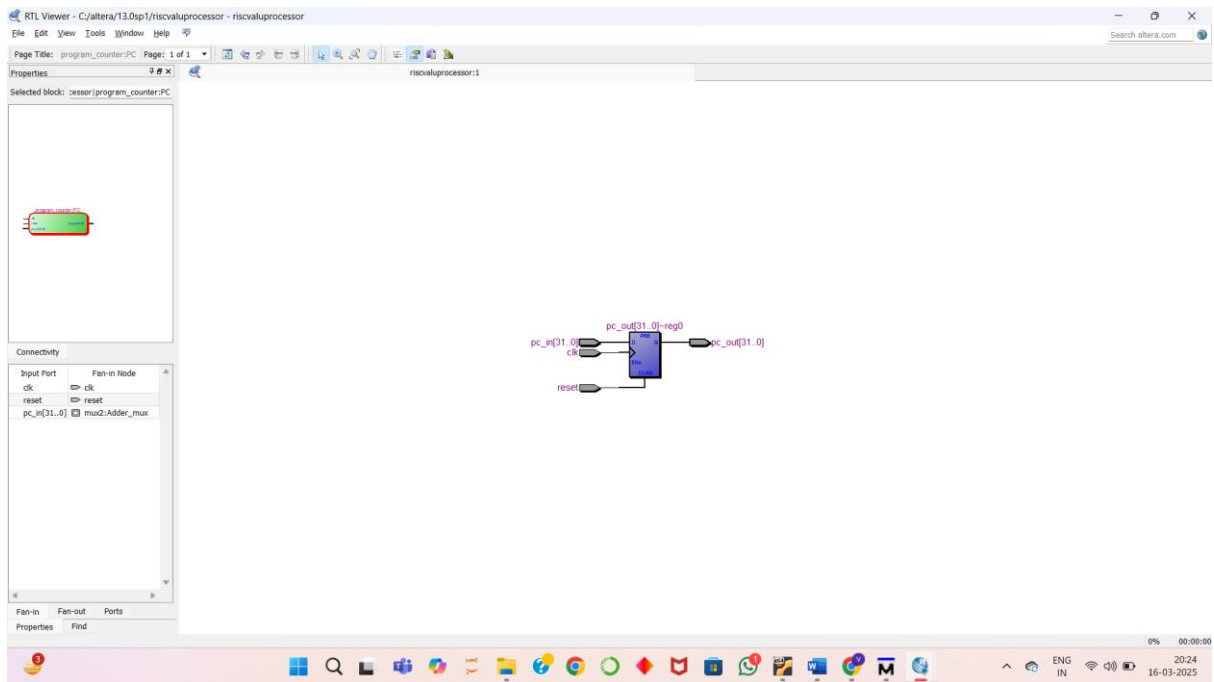


Fig. 16 RTL Unit of Program Counter.

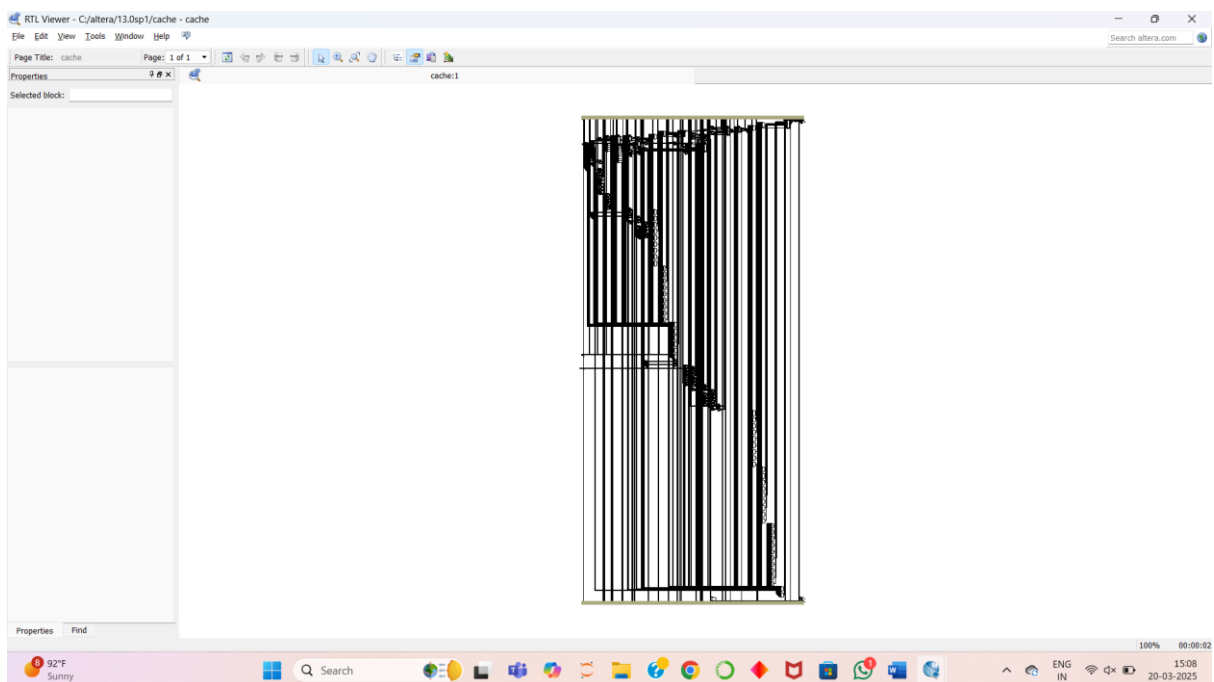


Fig.17 RTL of Cache

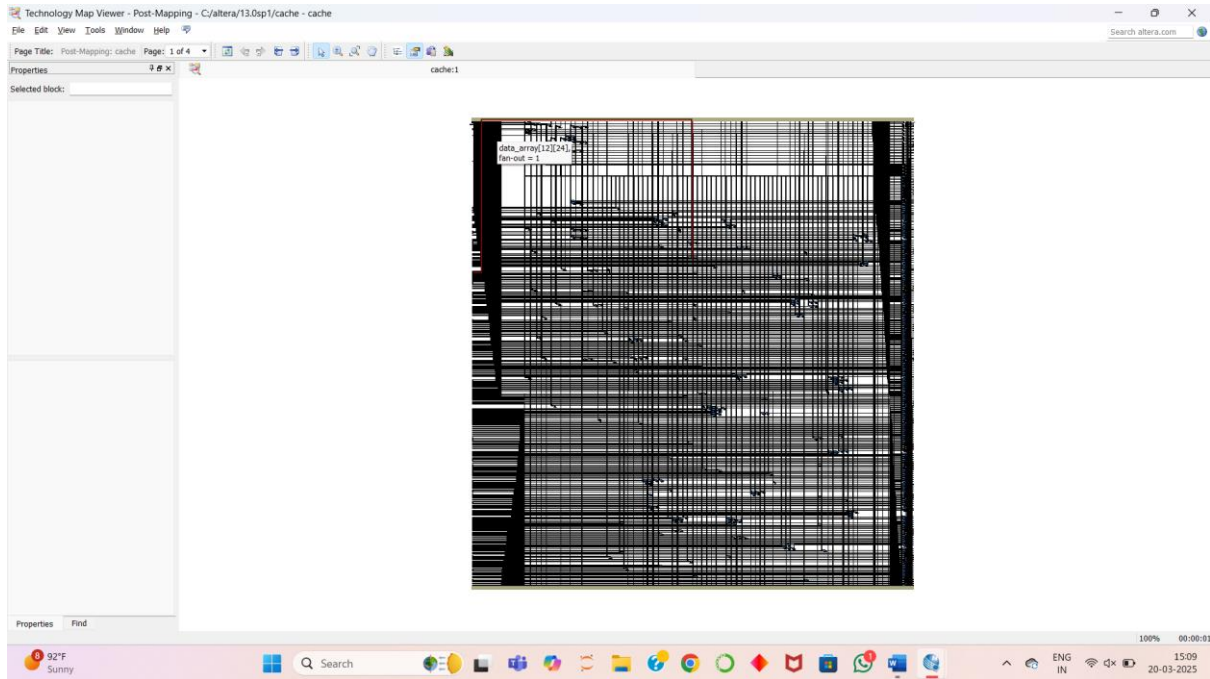


Fig.18 TTL of Cache

Conclusion – Here, after doing this project we got to know that how to implement, simulate RISC-V Processor along with Cache Management, how to integrate RISC-V Processor components with Cache (Instruction Cache) learnt also regarding Advantages and Disadvantages of RISC Processor with Cache, and how to improve them with several techniques present.

References - 1. <https://www.youtube.com/watch?v=dh88oe6O0QU&t=8823s> [1],

2. [\(The Morgan Kaufmann Series in Computer Architecture and Design\) David A. Patterson, John L. Hennessy - Computer Organization and Design RISC-V Edition The Hardware Software Interface-Morgan Kaufmann.pdf](#) [2]

3. [8. Cache Memory.pdf](#) [3]

Code in the Appendix –

```
module riscvpro1();
reg clk,reset;
riscvp_code uut(.clk(clk),.reset(reset));
initial begin
clk=0;
```

```
reset=1;
#5;
reset=0;
#400;
end
```

```
always begin
#5 clk=~clk;
end
endmodule
```

```
module riscvp_code(clk,reset);
input clk,reset;

wire
[31:0]pc_top,instruction_top,rd1_top,rd2_top,immext_top,mux1_top,sum_out_top,ne
xtopc_top,pcin_top,address_top,cache_data_out,writeback_top;

wire
regwrite_top,alusrc_top,zero_top,branch_top,sel2_top,memtoreg_top,memread_top,m
emwrite_top,hit_top,miss_top;

wire [1:0]aluop_top;
wire [3:0]control_top;
```

```
// Program Counter
```

```
program_counter PC(.clk(clk),.reset(reset),.pc_in(pcin_top),.pc_out(pc_top));
```

```
// Next to pc
```

```
pcplus4 PC_Adder(.frompc(pc_top),.nextopc(nextopc_top));
```

```
// Instruction Memory
```

```
instruction_memory
Inst_Memory(.clk(clk),.reset(reset),.read_address(pc_top),.instruction_out(instruction
_top));
```

```
// Reg file
```

```

reg_file
Reg_File(.clk(clk),.reset(reset),.regwrite(regwrite_top),.rs1(instruction_top[19:15]),.rs
2(instruction_top[24:20]),

.rd(instruction_top[11:7]),.write_data(writeback_top),.read_data1(rd1_top),.read_data
2(rd2_top));

```

```

// Imm. generator

```

```

immgen
ImmGen(.opcode(instruction_top[6:0]),.instruction(instruction_top),.immext(immext
_top));

```

```

// Control Unit

```

```

control_unit
Control_Unit(.instruction(instruction_top[6:0]),.branch(branch_top),.memread(memre
ad_top),.memtoreg(memtoreg_top),

.aluop(aluop_top),.memwrite(memwrite_top),.alusrc(alusrc_top),.regwrite(regwrite_t
op));

```

```

// Alu Control

```

```

alu_control
ALU_Control(.aluop(aluop_top),.fun7(instruction_top[30]),.fun3(instruction_top[14:
12]),.control_out(control_top));

```

```

// ALU

```

```

alu_unit
ALU(.a(rd1_top),.b(mux1_top),.control_in(control_top),.alu_result(address_top),.zero
(zero_top));

```

```

// Mux

```

```

mux1
ALU_Mux(.sel1(alusrc_top),.a1(rd2_top),.b1(immext_top),.mux1_out(mux1_top));

```

```

// Adder

```

```

adder Adder(.in_1(pc_top),.in_2(immext_top),.sum_out(sum_out_top));

```

```

// And_logic

```

```

and_logic And(.branch(branch_top),.zero(zero_top),.and_out(sel2_top));

```



```

// Mux2

mux2
Adder_mux(.sel2(sel2_top),.a2(nextopc_top),.b2(sum_out_top),.mux2_out(pcin_top))
;

// Data memory

data_memory      Data_mem(.clk(clk),.reset(reset),.memwrite(memwrite_top      &
miss_top),.memread(memread_top
miss_top),.read_address(address_top),.write_data(rd2_top),.memdata_out(cache_data
_out));

// Mux3

mux3
Memory_mux(.sel3(memtoreg_top),.a3(address_top),.b3(cache_data_out),.mux3_out(
writeback_top));

// Cache

cache
CACHE(.clk(clk),.reset(reset),.addr(address_top),.wdata(rd2_top),.mem_read(memre
ad_top),.mem_write(memwrite_top),.hit(hit_top),.miss(miss_top));

endmodule

module program_counter(clk,reset,pc_in,pc_out);
input clk,reset;
input [31:0]pc_in;
output reg [31:0]pc_out;
always@(posedge clk or posedge reset)
begin
if(reset)
pc_out<=32'b00;
else
pc_out<=pc_in;
end
end

```

```
endmodule
```

```
module pcplus4(frompc,nextopc);  
input [31:0]frompc;  
output [31:0]nextopc;  
assign nextopc=4+frompc;  
endmodule
```

```
module instruction_memory(clk,reset,read_address,instruction_out);  
input clk,reset;  
input [31:0]read_address;  
output [31:0]instruction_out;  
reg [31:0]imemory[63:0];  
integer k;
```

```
assign instruction_out=imemory[read_address];
```

```
always@(posedge clk or posedge reset)
```

```
begin
```

```
if(reset)
```

```
begin
```

```
for(k=0;k<64;k=k+1)
```

```
begin
```

```
imemory[k]=32'b00;
```

```
end
```

```
end
```

```
else
```

```
// R type
```

```
imemory[0]=32'h00000000;
```

```
imemory[4]=32'b00000000_11001_10000_000_01101_0110011;
```

```
imemory[8]=32'b0100000_00011_01000_000_00101_0110011;
```

```
imemory[12]=32'b00000000_00011_00010_111_00001_0110011;
```

```

memory[16]=32'b00000000_00101_00011_110_00100_0110011;

// I Type
memory[20]=32'b0000000000011_10101_000_10110_0010011;
memory[24]=32'b0000000000001_01000_110_01001_0010011;

// L type
memory[28]=32'b0000000001111_00101_010_01000_0000011;
memory[32]=32'b0000000000011_00011_010_01001_0000011;

// S type
memory[36]=32'b00000000_01111_00101_010_01100_0100011;
memory[40]=32'b00000000_01110_00110_010_01010_0100011;

// SB type
memory[44]=32'h00948663;

end
endmodule

// Cache Management
module cache(clk,reset,addr,wdata,mem_read,mem_write,rdata,hit,miss);
input clk,reset,mem_read,mem_write;
input [31:0]addr,wdata;
output reg [31:0]rdata;
output reg hit, miss; // 'hit' and 'miss' should be declared as 'reg' because they are
assigned inside 'always' block

parameter cache_size=16;
parameter index_bits=4;
parameter tag_bits=32-index_bits-2;

```

```
reg [tag_bits-1:0]tag_array[0:cache_size-1];
reg [31:0]data_array[0:cache_size-1];
reg valid[0:cache_size-1];

wire [tag_bits-1:0]tag=addr[31:index_bits+2];
wire [index_bits-1:0]index=addr[index_bits+1:2];
```

```
integer i;
always@(posedge clk)
begin
    if(reset)
    begin
        for(i=0;i<cache_size;i=i+1)
        begin
            valid[i]<=0;
            tag_array[i]<=0;
            data_array[i]<=0;
        end
    end

    else if(mem_read || mem_write)
    begin
        if(valid[index] && tag_array[index] == tag)
        begin
            hit<=1'b1;
            miss<=1'b0;
        end
        else
        begin
            hit<=1'b0;
            miss<=1'b1;
        end
    end
end
```

```

        tag_array[index]<=tag; // Fetch from memory in case of miss "DEADBEEF"
        data_array[index]<=32'hDEADBEEF;
        valid[index]<=1;
    end

    if(mem_read)
    begin
        rdata<=data_array[index];
    end

    if(mem_write)
    begin
        data_array[index]<=wdata;
    end
end

else
begin
    hit<=1'b0;
    miss<=1'b0;
end
end

endmodule

// Register File
module reg_file(clk,reset,regwrite,rs1,rs2,rd,write_data,read_data1,read_data2);
input clk,reset,regwrite;
input [4:0]rs1,rs2,rd;
input [31:0]write_data;
integer k;
reg [31:0]registers[31:0];
output [31:0]read_data1,read_data2;

```

initial begin

```
registers[0]=0;  
registers[1]=4;  
registers[2]=2;  
registers[3]=24;  
registers[4]=4;  
registers[5]=1;  
registers[6]=44;  
registers[7]=4;  
registers[8]=2;  
registers[9]=1;  
registers[10]=23;  
registers[11]=4;  
registers[12]=90;  
registers[13]=10;  
registers[14]=20;  
registers[15]=30;  
registers[16]=40;  
registers[17]=50;  
registers[18]=60;  
registers[19]=70;  
registers[20]=80;  
registers[21]=80;  
registers[22]=90;  
registers[23]=70;  
registers[24]=60;  
registers[25]=65;  
registers[26]=4;  
registers[27]=32;  
registers[28]=12;  
registers[29]=34;
```

```
    registers[30]=5;
    registers[31]=10;
end
```

```
always@(posedge clk)
begin
    if(reset)
    begin
        for(k=0;k<32;k=k+1)
        begin
            registers[k]<=32'b00;
        end
    end
    else if(regwrite)
    begin
        registers[rd]<=write_data;
    end
end
```

```
assign read_data1=registers[rs1];
assign read_data2=registers[rs2];
endmodule
```

```
module immgen(opcode,instruction,immext);
input [6:0]opcode;
input [31:0]instruction; // Fixed spelling mistake from "instuction" to "instruction"
output reg [31:0]immext;
always@(*)
begin
    case(opcode)
        7'b00000011:immext<={{20{instruction[31]}},instruction[31:20]}; // lw
```



```

    7'b0100011:immext<={{20{instruction[31]}},instruction[31:25],instruction[11:7]};
//sw

```

```

    7'b1100011:immext<={{19{instruction[31]}},instruction[31],instruction[30:25],instru
ction[11:8],1'b0}; // sb

```

```

    endcase

```

```

end

```

```

endmodule

```

```

module

```

```

    control_unit(instruction,branch,memread,memtoreg,aluop,memwrite,alusrc,regwrite);

```

```

    input [6:0]instruction;

```

```

    output reg branch,memread,memtoreg,memwrite,alusrc,regwrite;

```

```

    output reg [1:0]aluop;

```

```

    always@(*)

```

```

begin

```

```

    case(instruction)

```

```

        7'b0110011:    {alusrc,memtoreg,regwrite,memread,memwrite,branch,aluop}    <=
        8'b001000_10;

```

```

        7'b0000011:    {alusrc,memtoreg,regwrite,memread,memwrite,branch,aluop}    <=
        8'b111100_00;

```

```

        7'b0100011:    {alusrc,memtoreg,regwrite,memread,memwrite,branch,aluop}    <=
        8'b100010_00;

```

```

        7'b1100011:    {alusrc,memtoreg,regwrite,memread,memwrite,branch,aluop}    <=
        8'b000001_01;

```

```

    endcase

```

```

end

```

```

endmodule

```

```

module alu_unit(a,b,control_in,alu_result,zero);

```

```

    input [31:0]a,b;

```

```

    input [3:0]control_in;

```

```

    output reg zero;

```

```

    output reg [31:0]alu_result;

```

```

    always@(control_in or a or b)

```

```

begin
  case(control_in)
    4'b0000: begin zero<=0;alu_result<=a&b;end
    4'b0001: begin zero<=0;alu_result<=a|b;end
    4'b0010: begin zero<=0;alu_result<=a+b;end
    4'b0110: begin if(a==b) zero<=1; else zero<=0; alu_result<=a-b;end
    default: begin zero<=1'b0; alu_result<=32'b00;end
  endcase
end
endmodule

```

```

module alu_control(aluop,fun7,fun3,control_out);
input fun7;
input [2:0]fun3;
input [1:0]aluop;
output reg [3:0]control_out;
always@(*)
begin
  case({aluop,fun7,fun3})
    6'b00_0_000: control_out<=4'b0010;
    6'b01_0_000: control_out<=4'b0110;
    6'b10_0_000: control_out<=4'b0010;
    6'b10_1_000: control_out<=4'b0110;
    6'b10_0_111: control_out<=4'b0000;
    6'b10_0_110: control_out<=4'b0001;
  endcase
end
endmodule

```

```

module
data_memory(clk,reset,memwrite,memread,read_address,write_data,memdata_out);
input clk,reset,memwrite,memread;

```

```

input [31:0]read_address,write_data;
output [31:0]memdata_out;
integer k;
reg [31:0]d_memory[63:0];
always@(posedge clk or posedge reset)
begin
if(reset)
begin
for(k=0;k<64;k=k+1)
begin
d_memory[k]<=32'b00;
end
end
else if(memwrite)
begin
d_memory[read_address]<=write_data;
end
end
assign memdata_out=(memread)?d_memory[read_address]:32'b00;
endmodule

```

```

module mux1(sel1,a1,b1,mux1_out);
input sel1;
input [31:0]a1,b1;
output [31:0]mux1_out;
assign mux1_out=(sel1==1'b0)?a1:b1;
endmodule

```

```

module mux2(sel2,a2,b2,mux2_out);
input sel2;
input [31:0]a2,b2;
output [31:0]mux2_out;

```

```
assign mux2_out=(sel2==1'b0)?a2:b2;  
endmodule
```

```
module mux3(sel3,a3,b3,mux3_out);  
input sel3;  
input [31:0]a3,b3;  
output [31:0]mux3_out;  
assign mux3_out=(sel3==1'b0)?a3:b3;  
endmodule
```

```
module and_logic(branch,zero,and_out);  
input branch,zero;  
output and_out;  
assign and_out=branch&zero;  
endmodule
```

```
module adder(in_1,in_2,sum_out);  
input [31:0]in_1,in_2;  
output [31:0]sum_out;  
assign sum_out=in_1+in_2;  
endmodule
```